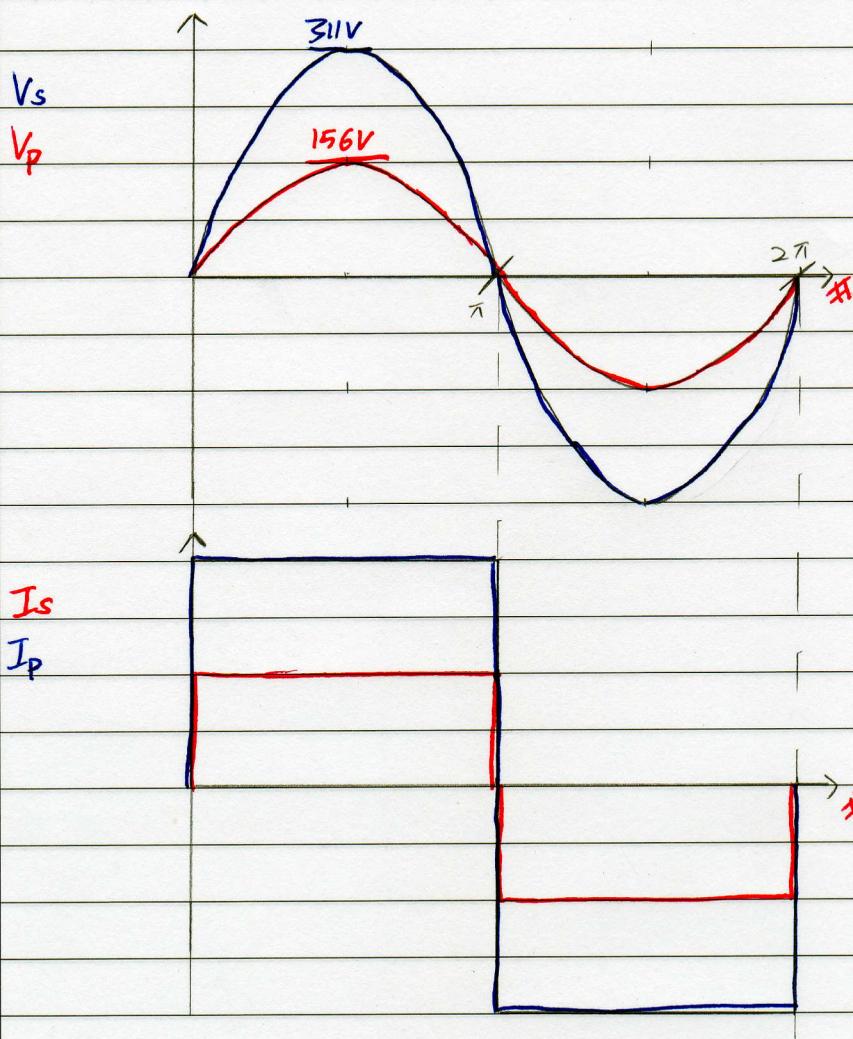


(a)



$$V_m = 220 \times \sqrt{2} = 311V$$

$$V_{pm} = V_m/2 = 156V$$

$$\text{Since } I_{D\text{peak}} = 10A \therefore I_{S\text{peak}} = 10A.$$

$$\text{Transformer Rating} = V_s I_s = (220) (10/\sqrt{2}) = 1.556 \text{ kVA}$$

$$PIV = V_m = 311V$$

$$I_{D\text{peak}} = 10A$$

$$I_{D\text{rms}} = I_{D\text{peak}} / \sqrt{2} = (10/\sqrt{2}) / \sqrt{2} = 5A$$

$$I_{D\text{avg}} = \frac{1}{2\pi} \int_0^{\pi} 10 \sin \omega d\omega = \frac{10}{2\pi} [-\cos \omega]_0^{\pi} = \frac{10}{\pi} = 3.18A$$

$$b) I_{o \text{ avg}} = 2 \times I_{o \text{ peak}} = 2 \times 3.18 A = 6.36 A$$

Under highly inductive,

$$I_{\text{rms}} = I_{\text{peak}} = I_{o \text{ avg}} = 6.36 A$$

$$\Rightarrow I_{\text{in peak}} = 6.36 A$$

$$a_n = a_0 = 0$$

$$b_n = \frac{1}{\pi} \int_0^{\pi} I_{\text{in}}(\omega t) \sin(n\omega t) dt = \frac{2}{\pi} \int_0^{\pi} 6.36 \sin(n\omega t) dt$$

$$= \frac{12.72}{\pi n} \left[-\cos(n\omega t) \right]_0^\pi = \frac{4.049}{n} [1 - (-1)^n]$$

$$\therefore I_{\text{in}} = \sum_{n=1}^{\infty} \frac{4.049}{n} [1 - (-1)^n] \sin(n\omega t) \quad \#$$

$$I_{\text{in rms}} = \left[\frac{4.049}{1} (2) \right] / \sqrt{2} = 5.726 A$$

$$I_{\text{in rms}} = 6.36 A$$

$$\text{THD} = \left[\left(\frac{I_{\text{in rms}}}{I_{\text{in rms}}} \right)^2 - 1 \right]^{\frac{1}{2}} = 48.34 \% \quad \#$$

$$\text{PF} = \frac{I_{\text{in rms}}}{I_{\text{in rms}}} \cos(\phi) = 0.9 \quad \#$$

$$\text{For purely resistive } \text{THD} = 0\% , \text{ PF} = 1 \quad \#$$

2a)

i) $V_{o \text{ arg}} = \frac{1}{2\pi} \int_0^{\pi} V_{o \text{ (acut)}} dt = \frac{2}{2\pi} \int_{\frac{\pi}{2}}^{\pi+\alpha} V_m \sin \omega t dt$

$$= \frac{V_m}{\pi} [\cos \omega t]_{\frac{\pi}{2}}^{\pi+\alpha} = \frac{2V_m}{\pi} \cos \alpha$$

$$\therefore \frac{2V_m}{\pi} \cos \alpha = 80V \Rightarrow \alpha = \cos^{-1}\left(\frac{80\pi}{2V_m}\right) \\ = 66.2^\circ \text{ } \cancel{x}$$

ii) $V_{o \text{ arg}} = 80V \cancel{x}$

$$V_{o \text{ rms}} = V_m / \sqrt{2} = 219.9V \cancel{x}$$

$$I_{o \text{ arg}} = V_{o \text{ arg}} / R = 16A \cancel{x}$$

$$I_{o \text{ rms}} = I_{o \text{ arg}} = 16A \cancel{x}$$

iii) $PIV = V_m = 311V \cancel{x}$

$$I_{T \text{ peak}} = 16A \cancel{x}$$


$$I_{T \text{ rms}} = I_{o \text{ rms}} / \sqrt{2} = 11.3A \cancel{x}$$

$$I_{T \text{ avg}} = I_{o \text{ avg}} / 2 = 8A \cancel{x}$$

iv) Transformer Rating = $V_s I_s = (311/\sqrt{2}) \times (I_{o \text{ rms}}) = 3.519 \text{ kVA } \cancel{x}$

b)

b)

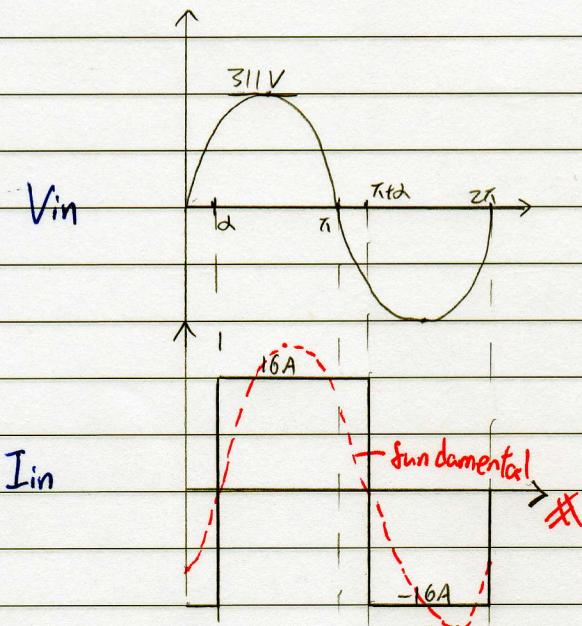

Phase shift: $I_{in(1)}$ lag by α

Find $I_{in(1)}$ peak:


$$I_{in(1) \text{ peak}} = \frac{1}{\pi} \frac{2}{\pi} \int_0^{\pi/2} 16 \sin(\omega t) dt = \frac{32}{\pi} [-\cos \omega t]_0^{\pi/2} = \frac{64}{\pi} A$$

$$I_{in(1) \text{ rms}} = I_{in(1) \text{ peak}} / \sqrt{2} = 14.405 A$$

$$PF = \frac{I_{in(1) \text{ rms}}}{16} \cos(\alpha) = 0.363 \times$$


3)

a)

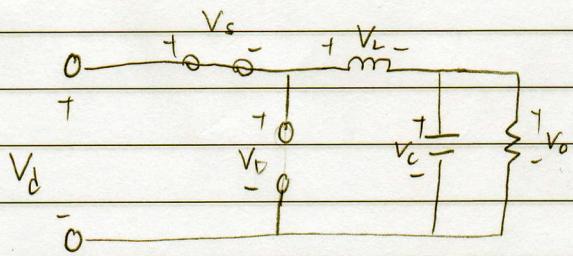

"On State"

A

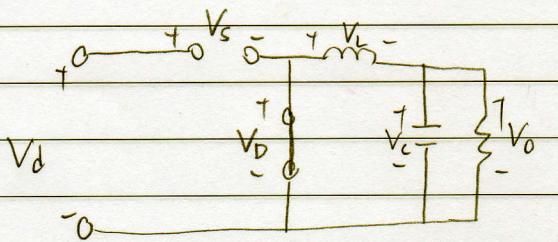

"Off State"

A

Under CCM:

$$\frac{V_o}{V_d} = D \text{ A}$$

b) $D = 0.6$

$$\frac{V_o}{V_d} = 0.6 \Rightarrow V_o = 50 \times 0.6 \\ = 30V \text{ A}$$

$$I_{o\arg} = V_{o\arg}/R = 30/25 \\ = 1.2A \text{ A}$$

$$I_{D\arg} = I_{o\arg} \times \frac{t_{off}}{T_S} = I_{o\arg} \times \frac{t_{off}}{T_S} = 1.2 \times (1 - 0.6) \\ = 0.48A \text{ A}$$

$$I_{S\arg} = I_{o\arg} \times \frac{t_{on}}{T_S} = I_{o\arg} \times \frac{t_{on}}{T_S} = 1.2 \times (0.6) \\ = 0.72A \text{ A}$$

c) Under BCM:

$$I_{oB} = \frac{1}{2} \Delta I_L, \quad \Delta I_L = \frac{V_o}{2} t_{off} = \frac{V_o}{2} (1-D) T_S$$

$$I_{oB} = \frac{V_o}{R} = \frac{V_o}{2L} (1-D) T_S \Rightarrow D = 1 - \frac{2L}{R T_S} = 0.2 \quad \text{X}$$

$$\Delta V_o = \frac{\Delta Q}{C}, \quad \Delta Q = \frac{1}{2} \times \frac{T_S}{2} \times \frac{\Delta I_L}{2}, \quad D = 0.2, \quad V_o = 10V$$

$$\Delta V_o = \frac{T_S^2 V_o (1-D)}{8 C L} = 0.1V \quad \text{X}$$

4)

a.) $f = f_s/m_f = 5000/100 = 50 \text{ Hz}$ ~~X~~

$$V_{o_1} = m_a \frac{V_d}{2} \sin(100\pi t)$$

$$V_{o_1, \text{rms}} = (m_a \frac{V_d}{2}) / \sqrt{2} = 229.8 \text{ V}$$

ii) for $m_a < 1$, the $V_{o_1, \text{rms}}$ is in linear region hence is easy to control the voltage. When $m_a > 1$, it is in non linear region hence not easy to control. ~~X~~


b.) $Z_1 = \sqrt{R^2 + (2\pi f_i L)^2} = \sqrt{(40)^2 + (100\pi \times 95.5 \times 10^{-3})^2} = 50 \Omega$

$$I_{o, \text{rms}} = V_{o, \text{rms}} / Z_1 = 4.596 \text{ A}$$


$$\phi = \tan^{-1} \left(\frac{2\pi f_i L}{R} \right) = 36.87^\circ$$

$$\text{PF} = \cos(\phi) = 0.8 \text{ lag}$$

ii)

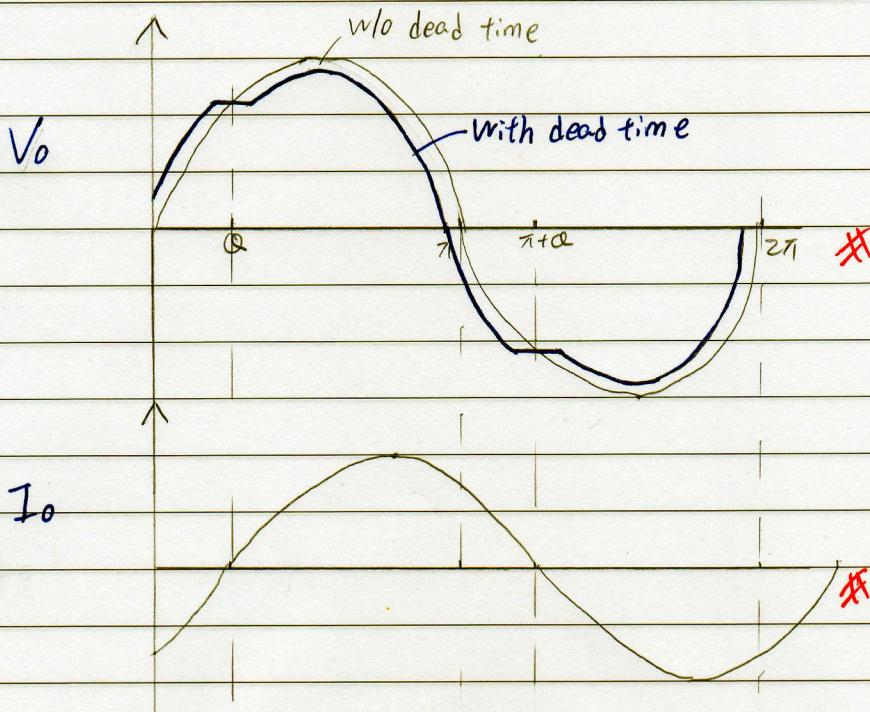

(i)

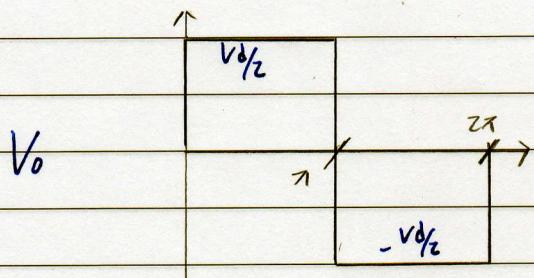

$$a_n = a_0 = 0$$

$$b_n = \frac{1}{\pi} \int_0^{2\pi} V_o(\text{ave}) \sin(nwt) dt = \frac{2}{\pi} \int_0^{\pi} \frac{V_d}{2} \sin(nwt) dt$$

$$= \frac{V_d}{\pi n} \left[-\cos(nwt) \right]_0^{\pi} = \frac{V_d}{n\pi} [1 - (-1)^n]$$

$$\therefore V_o = \sum_{n=1}^{\infty} \frac{V_d}{n\pi} [1 - (-1)^n] \sin(nwt) \quad \#$$

$$\text{ii)} \quad V_{o3} = \frac{V_d}{3\pi} [1 - (-1)^{\frac{3}{2}}] = 169.8V$$

$$V_{o3 \text{ rms}} = V_{o3} / \sqrt{2} = 120V \quad \#$$