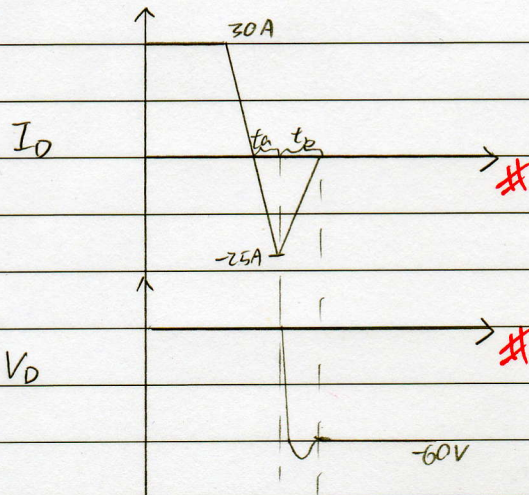


1a)



ii) $SF = t_b/t_a$, $t_b + t_a = t_{rr}$, $I_{rr} = \frac{di}{dt} \times t_a$



$$t_a = I_{rr} / \left[\frac{di}{dt} \right] = 25/12 = 2.083 \mu s$$

$$t_b = SF \times t_a = 0.6 \times 2.083 = 1.25 \mu s$$

$$t_{rr} = t_b + t_a = 3.333 \mu s$$

Since SF is $< 1 \therefore$ use fast recovery diode.

b)

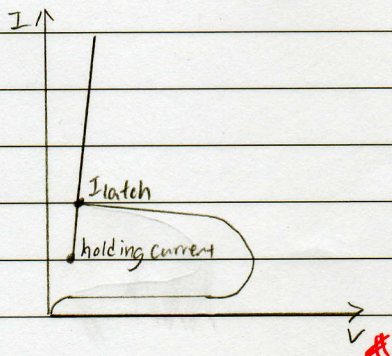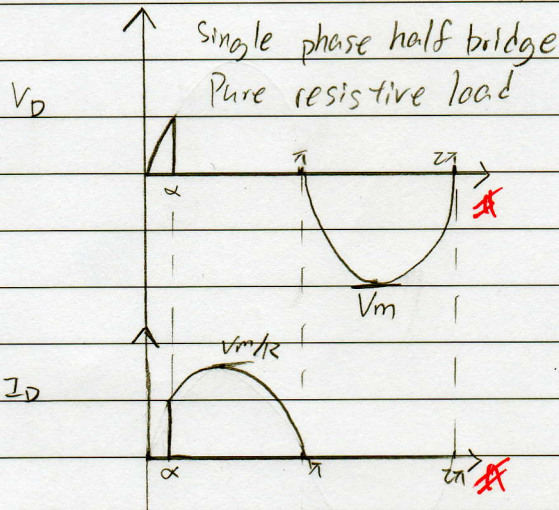

2) Highly inductive, $V_o \text{ avg} = 190 \text{ V}$, $R = 12 \Omega$, $V_m = \sqrt{2} \times 220 \text{ V}$

a) $I_{\text{rms}} = I_{\text{peak}} = I_o \text{ avg} = V_o \text{ avg} / R = 15.833 \text{ A}$


ii)
$$V_o \text{ avg} = \frac{1}{2\pi} \int_0^{2\pi} V_o(\omega t) d\omega t = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t d\omega t$$

$$= \frac{V_m}{\pi} [-\cos \omega t]_{\alpha}^{\pi+\alpha}$$

$$= \frac{2V_m}{\pi} \cos \alpha$$

$\Rightarrow \frac{2V_m}{\pi} \cos \alpha = 190 \text{ V} \Rightarrow \alpha = 16.4^\circ$

iii)

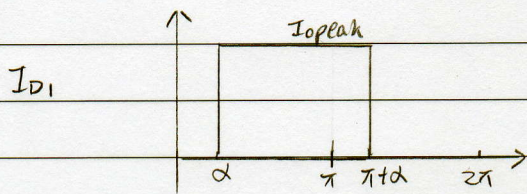

$PIV = V_m = 311 \text{ V}$

$I_{D1 \text{ avg}} = I_o \text{ avg} / 2 = 7.9165 \text{ A}$

$I_{D1 \text{ rms}} = I_{\text{rms}} \times \sqrt{\frac{1}{2}} = 11.2 \text{ A}$

$I_{D1 \text{ peak}} = I_{\text{peak}} = 15.833 \text{ A}$


b) $V_{\text{in rms}} = 220 \text{ V}$

$I_{\text{in rms}} = I_{D1 \text{ rms}} \times \sqrt{2} = 15.833 \text{ A}$


Transformer kVA = $V_{\text{in rms}} \times I_{\text{in rms}} = 3.483 \text{ kVA}$

c)


V_o w/o FHD

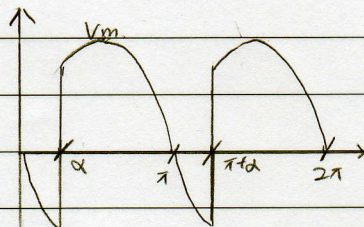


V_o with FHD, for resistive & inductive

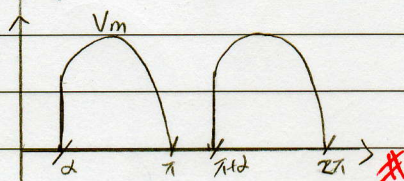


I_o for inductive

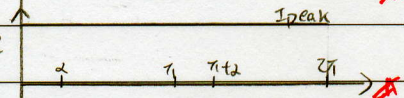


I_s for inductive

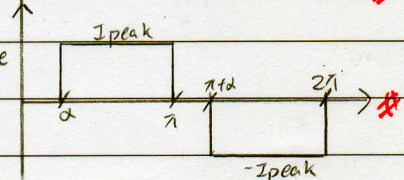


I_o for resistive

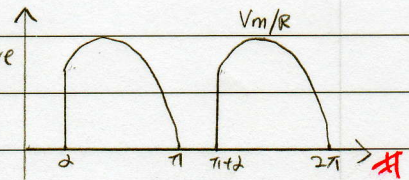

I_s for resistive

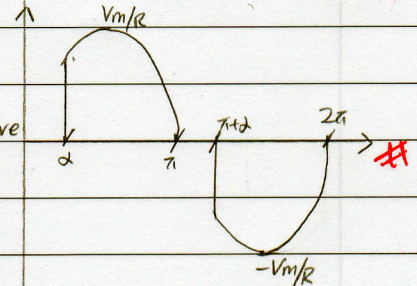


3)

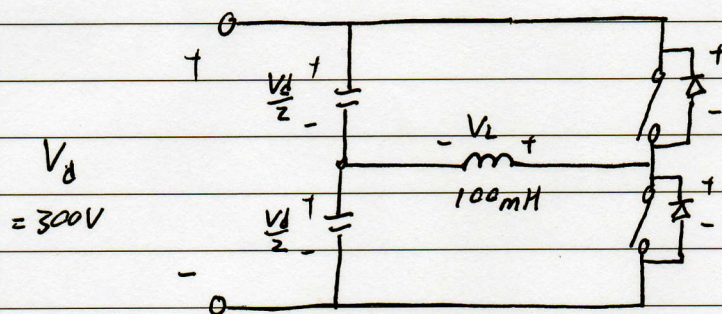

$$f = 50 \text{ Hz}$$

$$T_s = 0.02 \text{ s}$$

a)

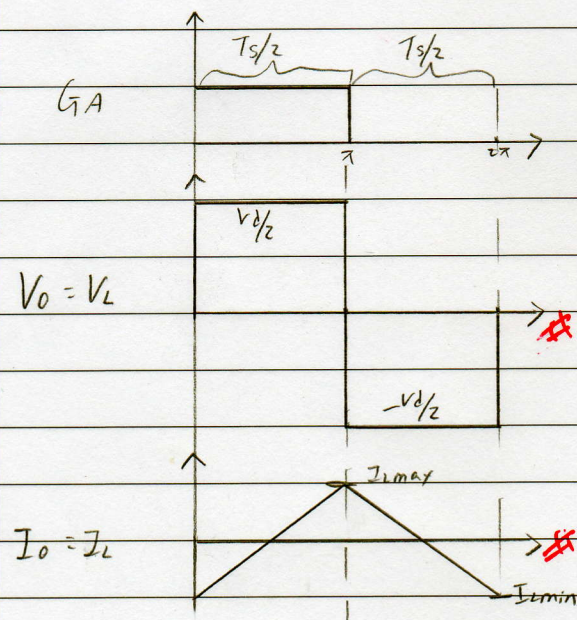

$$\begin{aligned} \Delta I_L &= \left(\frac{V_d}{2} \right) / L \cdot t_{on} \\ &= \frac{V_d}{2L} \times T_s / 2 \\ &= 15 \text{ A} \end{aligned}$$

$$I_{Lmax} = \Delta I_L / 2 = 7.5 \text{ A}$$

$$I_{Lmin} = -\Delta I_L / 2 = -7.5 \text{ A}$$

ii) $V_{rms} = V_d / 2 = 150 \text{ V}$

$$Z = 2\pi fL = 31.42 \Omega$$

$$I_{orms} = V_{rms} / Z = 4.775 \text{ A}$$

b) V_o fundamental frequency = 50 Hz

On state $V_{load} = 0 \text{ V}$


Off state $V_{load} = 300 \text{ V}$

$$V_{load} = \frac{300}{2} \times m_a \sin(100\omega t) + \frac{300}{2}$$


For max V_{load} , $m_a = 1$

$$\therefore V_{load \text{ peak max}} = \frac{300}{2} \text{ V} + \text{offset} = \frac{300}{2} + \frac{300}{2} = 300 \text{ V}$$

4)

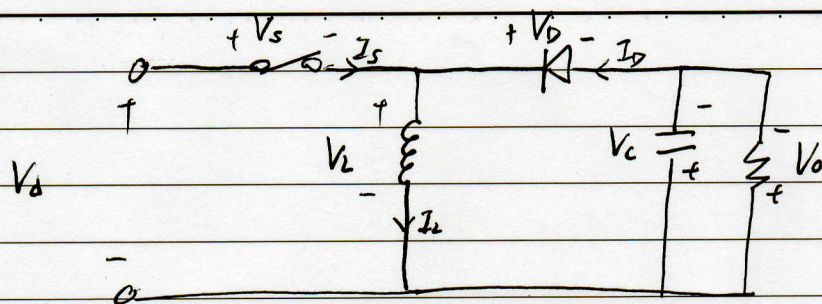

a)

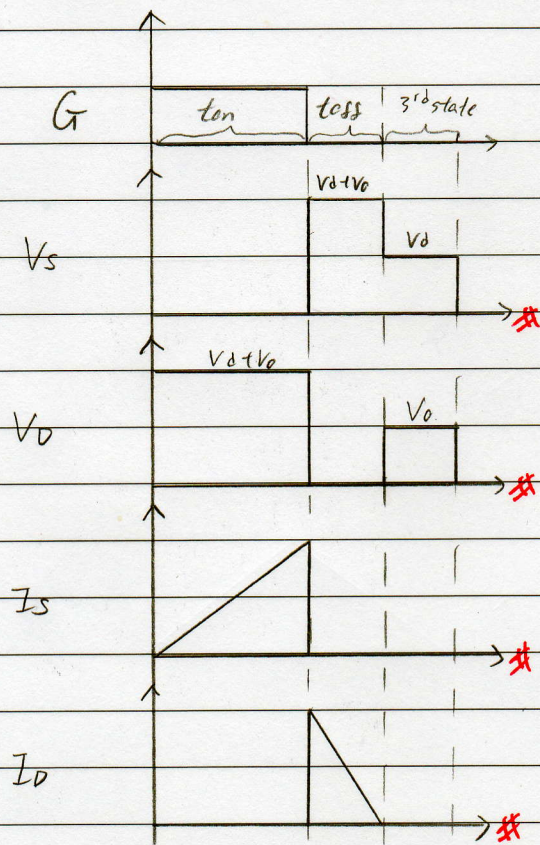

b) Large amount of Power is require to start an induction motor, if voltage remain, there will be large initial current which may damage the motor. Hence by using voltage boost, initial current will be reduced. ~~✗~~

c) Varying stator frequency will reduce the magnetic flux generated, hence lowering the motor speed. ~~✗~~