

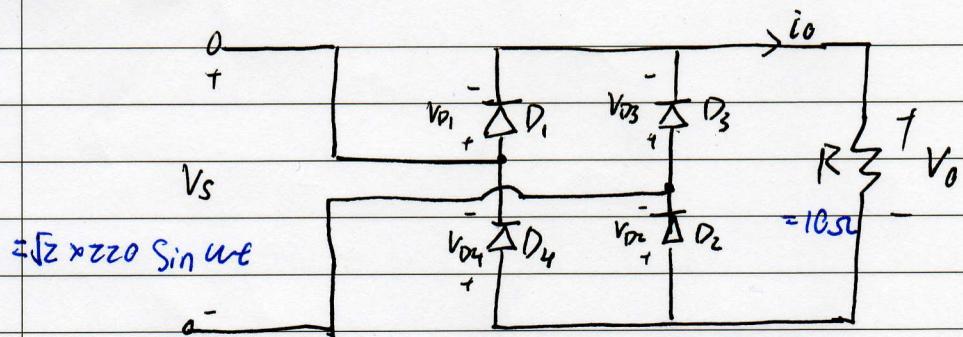


i)

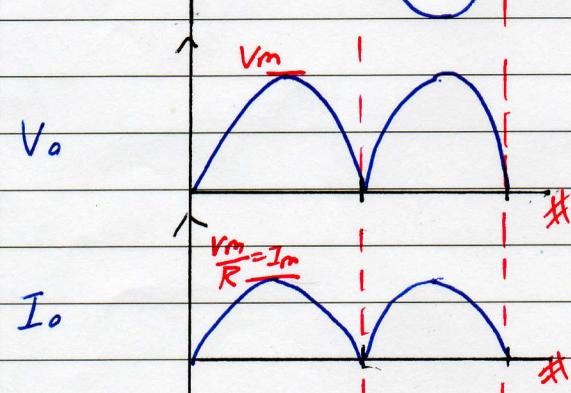

Phase

Pure Resistive

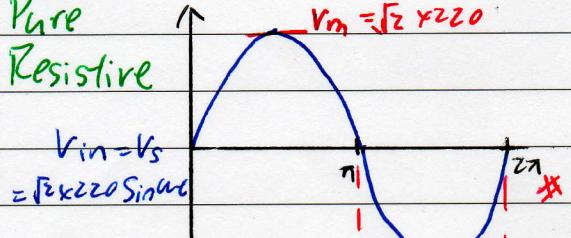

I_o

$$V_{rms} = V_m / \sqrt{2}$$

$$= 220 V \text{ #}$$

$$I_{rms} = (V_m / R) / \sqrt{2}$$

$$= 22 A \text{ #} \Rightarrow V_{rms} / R$$

$$V_o \text{ arg} = \frac{1}{2\pi} \int_0^{2\pi} V_o \text{ (pure) } dt$$

$$= \frac{2}{2\pi} \int_0^{\pi} V_o \sin \omega t \, dt$$

$$= \frac{V_m}{\pi} [-\cos \omega t]_0^\pi$$

$$= \frac{2}{\pi} V_m = 198.07 V \text{ #}$$

$$I_o \text{ arg} = V_o \text{ arg} / R$$

$$= 19.807 A \text{ #}$$

ii)

I_in

$$V_m = 311.127 V$$

$$I_m = 31.1127 A$$

iii)

V_D4, V_D3

$$V_{in rms} = 220 V$$

$$I_{in rms} = I_m / \sqrt{2} = 22 A$$

$$\text{Transformer Rating} = V_{in rms} \times I_{in rms} = 4840 \text{ VA} \text{ #}$$



V_D1, V_D2

$$PIV = V_m = 311.127 V \text{ #}$$


$$I_o \text{ peak} = I_m = 31.1127 A \text{ #}$$

$$I_o \text{ arg} = I_o \text{ peak} / 2 = 9.9035 A \text{ #}$$
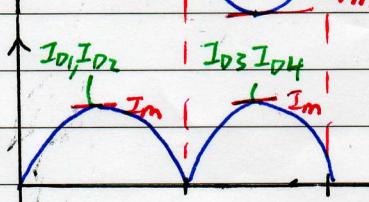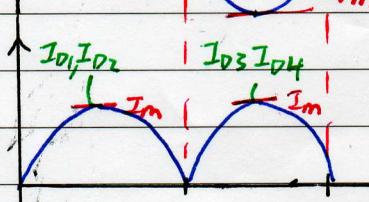
$$I_o \text{ rms} = I_o \text{ peak} \times \frac{1}{2} = 15.556 A \text{ #}$$



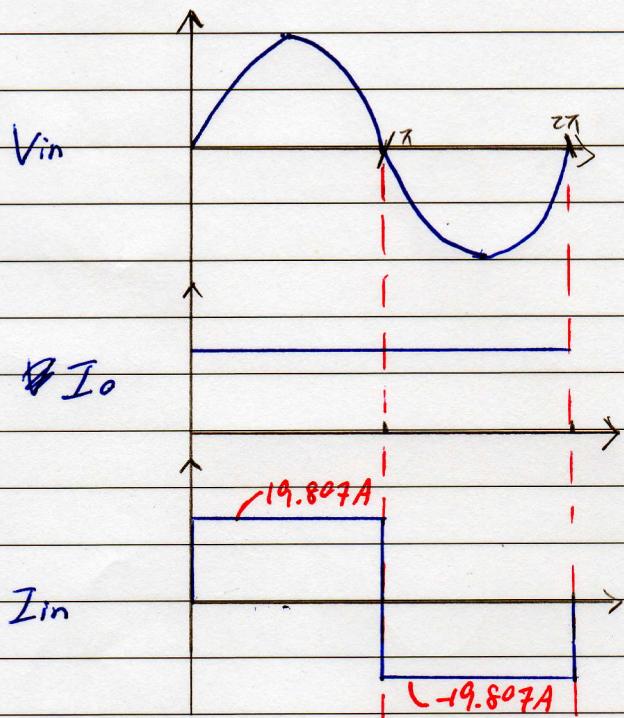b) For high inductive load, I_o is constant, all voltage wave no change



$$I_{o\text{rms}} = I_{o\text{peak}} = I_{o\text{avg}}$$

$$I_{o\text{avg}} = V_{o\text{avg}} / R = 19.807 \text{ A}$$


$$V_{in\text{rms}} = 220 \text{ V}$$

$$I_{in\text{rms}} = 19.807 \text{ A}$$

$$\begin{aligned} \text{Transformer Rating} &= V_{in\text{rms}} \times I_{in\text{rms}} \\ &= 4357.54 \text{ VA} \end{aligned}$$

$$2) V_{L1 \text{ rms}} = 220V, V_{L1 \text{ m}} = 220 \times \sqrt{2} \times \sqrt{3} = 538.89V$$

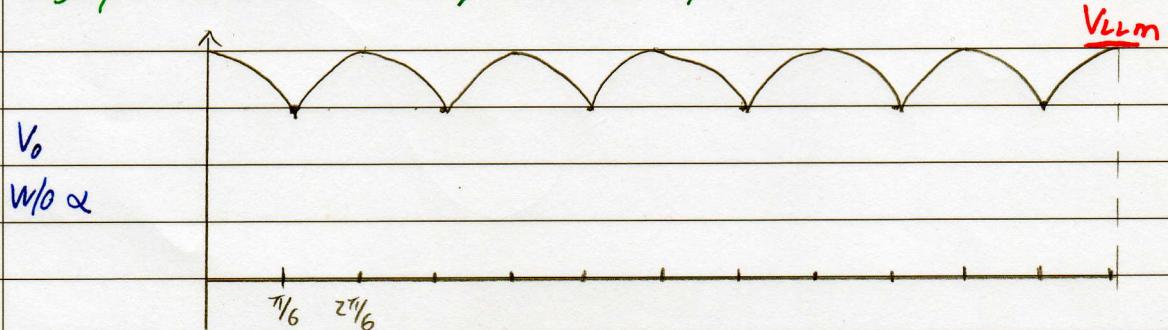
Highly inductive load, $R = 10\Omega$, $f = 50\text{Hz}$



When $\alpha = 0$, $V_o \text{ arg}$ is max.


$$\begin{aligned} V_o \text{ arg} &= \frac{1}{2\pi} \int_0^{2\pi} V_o \cos(\omega t) dt = \frac{1}{2\pi} \times 12 \times V_{L1 \text{ m}} \int_0^{\pi/6} \cos(\omega t) dt \\ &= \frac{6}{\pi} V_{L1 \text{ m}} [\sin(\omega t)]_0^{\pi/6} = \frac{3}{\pi} V_{L1 \text{ m}} = 514.6V \end{aligned}$$

a)

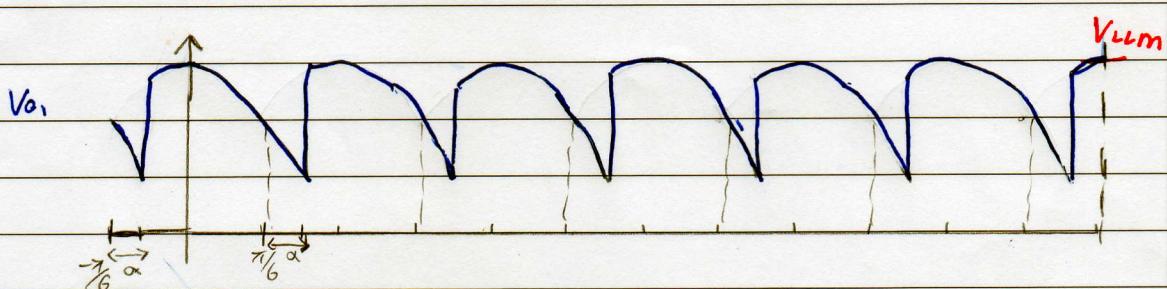

$$V_{o1 \text{ arg}} = 80\% V_o \text{ arg} = 411.68V$$
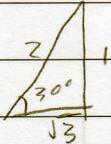
$$V_{o1 \text{ arg}} = \frac{1}{2\pi} \int_0^{2\pi} V_{o1} \cos(\omega t) dt = \frac{1}{2\pi} \times 6 \int_{-\pi/6+\alpha}^{\pi/6+\alpha} V_{L1 \text{ m}} \cos(\omega t) dt$$



$$= \frac{3}{\pi} V_{L1 \text{ m}} \left[\sin\left(\frac{\pi}{6} + \alpha\right) - \sin\left(-\frac{\pi}{6} + \alpha\right) \right]$$

$$= \frac{3}{\pi} V_{L1 \text{ m}} \left[\sin\left(\frac{\pi}{6}\right) \cos(\alpha) + \cos\left(\frac{\pi}{6}\right) \sin(\alpha) - \sin(\alpha) \cos\left(\frac{\pi}{6}\right) + \cos(\alpha) \sin\left(\frac{\pi}{6}\right) \right]$$

$$= \frac{3}{\pi} V_{L1 \text{ m}} \left[\frac{1}{2} \cos(\alpha) + \frac{\sqrt{3}}{2} \sin(\alpha) + \frac{1}{2} \cos(\alpha) \right] = \frac{3}{\pi} V_{L1 \text{ m}} \cos(\alpha)$$

$$\frac{3}{\pi} V_{L1 \text{ m}} \cos(\alpha) = 411.68 \Rightarrow \alpha = 36.87^\circ \text{ } \cancel{\text{X}}$$

ii) $I_{o1, \text{arg}} = V_{o1, \text{arg}} / R = 41.168 A$

$I_{o1, \text{rms}} = I_{o1, \text{peak}} = I_{o1, \text{arg}} = 41.168 A$ (highly inductive)

iii) Since each thyristor conduct for 2 pulses out of 6 pulses,

$$\therefore I_{T1, \text{avg}} = I_{o1, \text{arg}} \times \frac{2}{6} = 13.723 A$$

$$I_{T1, \text{rms}} = I_{o1, \text{rms}} \times \sqrt{\frac{2}{6}} = 23.768 A$$

iv) $P_{o1, \text{arg}} = V_{o1, \text{arg}} \times I_{o1, \text{arg}} = 16.948 \text{ kVA}$

$P_{in, \text{rms}} = V_{in, \text{rms}} \times I_{in, \text{rms}}$ (Per phase)

$V_{in, \text{rms}} = 220 V$

$$I_{in, \text{rms}} = I_{o1, \text{rms}} \times \sqrt{\frac{4}{6}} = 33.613 A$$


$P_{in, \text{rms}} = 7.395 \text{ kVA}$

$$TUF = \frac{P_{o1, \text{arg}}}{3 P_{in, \text{rms}}} = 76.39\%$$


v) Transformer rating = $3 P_{in, \text{rms}} = 22.185 \text{ kVA}$

$$\begin{aligned} \text{Transformer Actual rating} &= \frac{1}{0.8} \times 22.185 \text{ kVA} \\ &= 27.73 \text{ kVA} \end{aligned}$$

b)

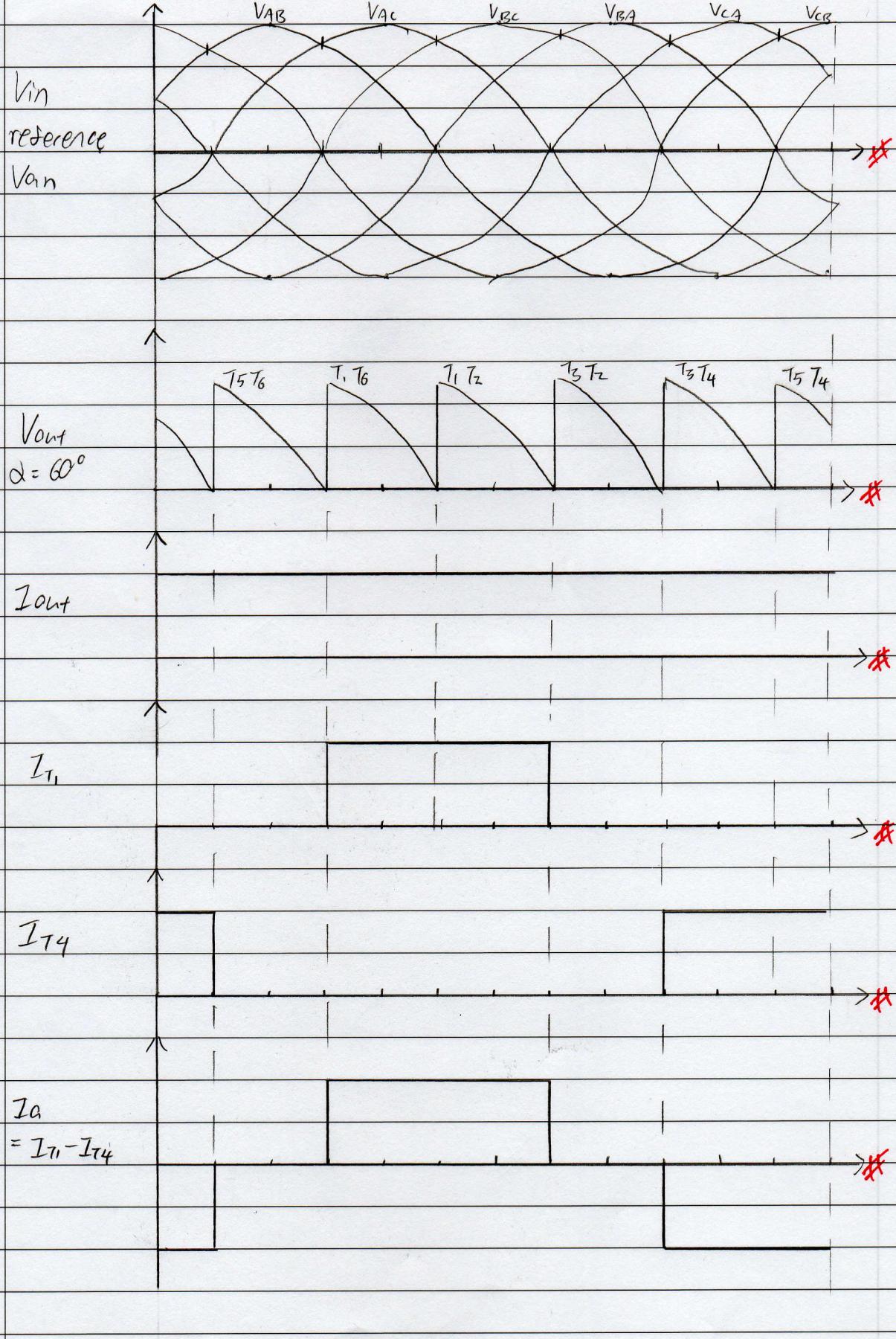

3) Buck:

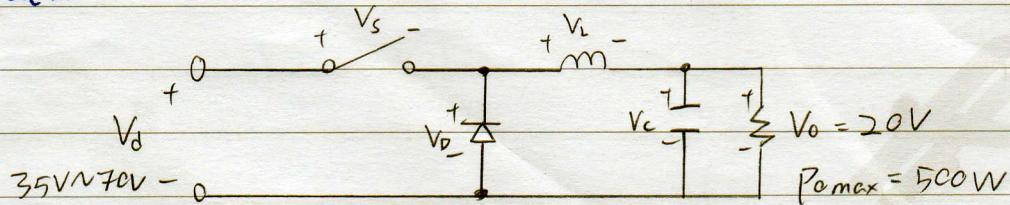


$$\text{CCM: } P_{o\min} = 5\% P_{o\max} = 25\text{W}$$

$$f_s = 100\text{kHz} \Rightarrow T_s = 0.01\text{ms}$$

$$\Delta V_o \leq 200\text{mV}$$

$$P_o = P_{in}, V_{i\text{avg}} = 0V, I_{c\text{ avg}} = 0A$$

a)

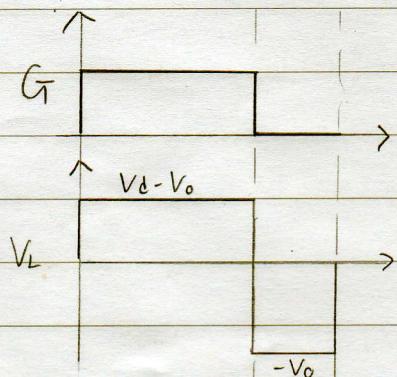

$$[V_d - V_o]_{ton} + [-V_o]_{toff} = 0$$

$$V_d t_{on} = V_o (t_{on} + t_{off})$$

$$t_{on} = D T_s, t_{on} + t_{off} = T_s$$

$$V_d D T_s = V_o T_s$$

$$\Rightarrow \frac{V_o}{V_d} = D \quad (\text{prove})$$

$$P_o = V_o I_o = V_d I_d$$

$$\Rightarrow \frac{V_o}{V_d} = \frac{I_o}{I_d} = D \quad \therefore \frac{I_o}{I_d} = \frac{1}{D} \quad (\text{prove})$$

When $V_d = 40V, P_o = 500\text{W}, V_o = 20V$:

$$D = \frac{V_o}{V_d} = \frac{20}{40} = 0.5 \quad \text{**}$$

$$I_o = \frac{P_o}{V_o} = 25A \quad \text{**}$$


$$I_d = I_o D = 12.5A \quad \text{**}$$

Home ad found $\Delta I_L = \text{end ad found}, \text{Home ad of } \Delta I_L$

$$\frac{\sum_{n=1}^{100} 0.005}{0.5} = \frac{(0.5-1) \times \sum_{n=1}^{100} 10.0}{0.5 \times 10.0 \times 100 \times 0.5 \times 8} = \frac{(-0.5) \times 500}{500} = -0.5 = 0.5 \text{ A}$$

$$F(0.5) = 1.21 \quad \text{**}$$

b) At BCM:

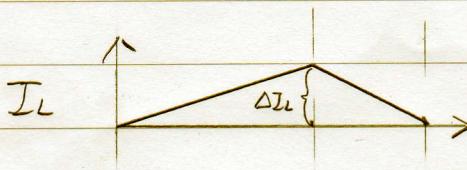

$$I_L = I_C + I_O$$

$$I_{L_B} = I_{O_B} = \frac{1}{2} \times T_S \times \Delta I_L / T_S = \frac{1}{2} \Delta I_L$$

$$\Delta I_L = \frac{V_o}{2} (1-D) T_S$$

$$I_{O_B} = \frac{\frac{V_o (1-D) T_S}{2}}{2L} = \frac{V_o}{R_B} \Rightarrow L = \frac{(1-D) R_B}{2 f_s} \text{ (prove)} \quad \text{X}$$

$$\text{For } V_d = 35V \sim 70V, V_o = 20V \Rightarrow D = \frac{20}{35} \sim \frac{20}{70}$$


$$\text{Under BCM, } P_{\min} = 25W \Rightarrow R_B = \frac{V_o^2}{P_{\min}} = 16\Omega$$

To guarantee CCM, L must be large $\Rightarrow D$ must be small

$$L = \frac{(1-D) R_B}{2 f_s} = \frac{\left(1 - \frac{20}{70}\right) \times 16}{2 \times 100 \times 10^3} = 57.143 \mu H \quad \text{X}$$

$$c) \Delta V_o = \frac{\Delta \alpha}{C} = \frac{1}{C} \left[\frac{1}{2} \times T_S \times \frac{\Delta I_L}{2} \right] = \frac{V_o (1-D) T_S^2}{8LC}$$
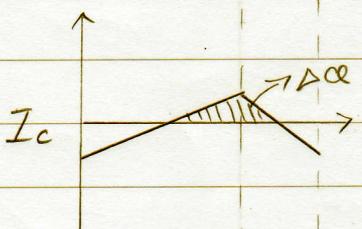
$$\Rightarrow \frac{\Delta V_o}{V_o} = \frac{T_S^2}{8LC} (1-D) \text{ prove X}$$



$$\Delta V_o \leq 200mV,$$


For ΔV_o to be small, C must be big $\Rightarrow D$ must be small

$$\frac{\Delta V_o}{V_o} = \frac{T_S^2}{8LC} (1-D) = \frac{(0.01 \times 10^{-3})^2 \times (1 - \frac{20}{70})}{8 \times 57.143 \times 10^{-6} \times C} = \frac{200 \times 10^{-3}}{20}$$

$$\Rightarrow C = 15.625 \mu F \quad \text{X}$$

FINISH STRONG!

4)

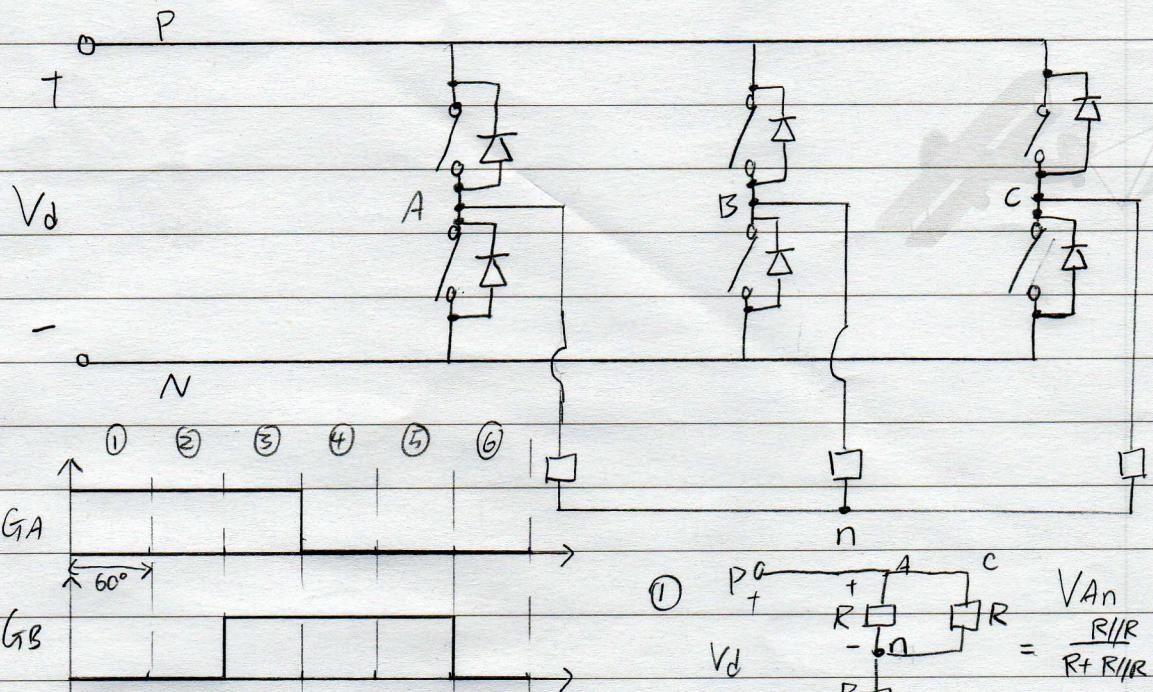


$$\textcircled{1} \quad P_A^o = \frac{V_{An}}{R//R} = \frac{R//R}{R+R//R} \times V_d = \frac{1}{3} V_d$$

$$\textcircled{2} \quad P_B^o = \frac{V_{An}}{R} = \frac{R}{R+R//R} V_d = \frac{2}{3} V_d$$

$$\textcircled{3} \quad P_C^o = \frac{V_{An}}{R//R} = \frac{R//R}{R+R//R} V_d = \frac{1}{3} V_d$$

a)

$$V_{AB} = V_{An} - V_{Bn}$$

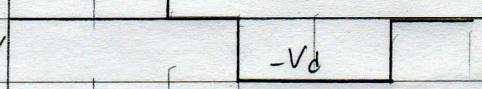

$$\frac{1}{3} V_d$$

$$V_{An}$$

~~*~~



$$\textcircled{4} \quad P_B^o = \frac{V_{An}}{R} = -V_d \frac{R//R}{R+R//R} = -\frac{2}{3} V_d$$

$$\textcircled{5} \quad P_C^o = \frac{V_{An}}{R//R} = -V_d \frac{R}{R+R//R} = -\frac{1}{3} V_d$$

$$\textcircled{6} \quad P_A^o = \frac{V_{An}}{R//R} = -V_d \frac{R//R}{R+R//R} = -\frac{1}{3} V_d$$

FINISH STRONG!

b)

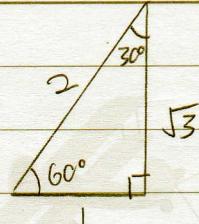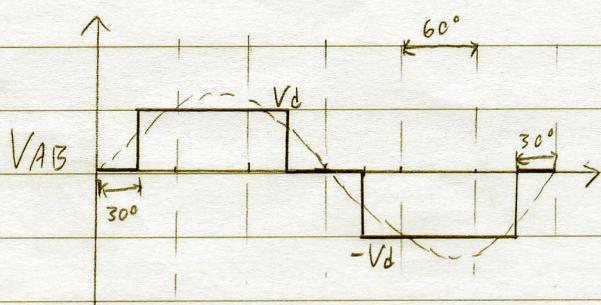

$$\cos\left(\frac{5\pi}{6}\right) = -\cos\left(\frac{5\pi}{6} - \frac{6\pi}{6}\right)$$

$$= -\cos(-\frac{\pi}{6})$$

$$= -\cos(\frac{\pi}{6})$$

$$= -\frac{\sqrt{3}}{2}$$

Since finding fundamental, set $n=1$

$$b_1 = \frac{1}{\pi} \int_0^{2\pi} V_{AB} \sin(\omega t) dt = \frac{2}{\pi} \int_{\pi/6}^{5\pi/6} V_d \sin(\omega t) dt = \frac{2V_d}{\pi} [-\cos(\omega t)]_{\pi/6}^{5\pi/6}$$

$$= \frac{2V_d}{\pi} [\cos(\frac{\pi}{6}) - \cos(\frac{5\pi}{6})] = \frac{2V_d}{\pi} \left[\frac{\sqrt{3}}{2} + \frac{\sqrt{3}}{2} \right] = \frac{2\sqrt{3}}{\pi} V_d$$

$$b_1 = V_{AB \text{ peak}} \Rightarrow V_{AB \text{ rms}} = \frac{V_{AB \text{ peak}}}{\sqrt{2}} = \frac{2\sqrt{3}}{\sqrt{2}\pi} V_d = \frac{2\sqrt{2}\sqrt{3}}{\sqrt{2}\sqrt{2}\pi} V_d = \frac{2}{2} \frac{\sqrt{2}\sqrt{3}}{\pi} V_d = \frac{\sqrt{6}}{\pi} V_d \text{ (prove)}$$

$$b_1 = \frac{1}{\pi} \int_0^{2\pi} V_{An} \sin(\omega t) dt = \frac{4}{\pi} \int_0^{\pi/3} \frac{1}{3} V_d \sin(\omega t) dt + \frac{2}{\pi} \int_{\pi/3}^{2\pi/3} \frac{2}{3} V_d \sin(\omega t) dt$$

$$= \frac{4V_d}{3\pi} [-\cos(\omega t)]_0^{\pi/3} + \frac{4V_d}{3\pi} [-\cos(\omega t)]_{\pi/3}^{2\pi/3}$$

$$\cos^2 \frac{\pi}{3} = -\cos(\frac{2\pi}{3} - \frac{3\pi}{3})$$

$$= -\cos(-\frac{\pi}{3})$$

$$= -\cos \frac{\pi}{3}$$

$$= -\frac{1}{2}$$

$$= \frac{4V_d}{3\pi} [1 - \cos \frac{\pi}{3} - \cos^2 \frac{\pi}{3} + \cos \frac{\pi}{3}]$$

$$= \frac{4V_d}{3\pi} \left[\frac{3}{2} \right]$$

$$= \frac{2}{\pi} V_d$$

$$b_1 = V_{An \text{ peak}} \Rightarrow V_{An \text{ rms}} = \frac{V_{An \text{ peak}}}{\sqrt{2}} = \frac{2}{\sqrt{2}\pi} V_d = \frac{\sqrt{2} \cdot 2}{\pi \sqrt{2} \sqrt{2}} V_d = \frac{2}{2} \frac{\sqrt{2}}{\pi} V_d = \frac{\sqrt{2}}{\pi} V_d \text{ (prove)}$$

#

c) -